

Indian Institute of Information Technology Chittoor, Sri City

Name of the Exam: Digital and Electrical Circuits Duration: 3 hours

Max. Marks: 100


Roll No.: _____ Room No.: _____ Seat No.: _____

Name: _____ Invigilator's Signature: _____



- Instructions:
1. This is a closed book exam
 2. Scientific/Basic Calculators allowed
 3. Attach question paper with answer sheet

{Questions 1-15 carry 6 marks each, MCQ's carry 1 mark each}

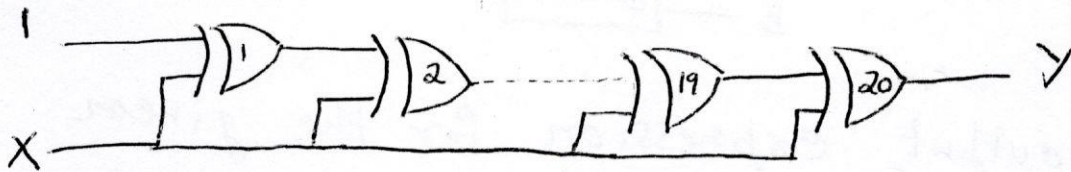- 1) a] The given circuit consists of cascade of 20 XOR gates. Determine the expression for output Y.



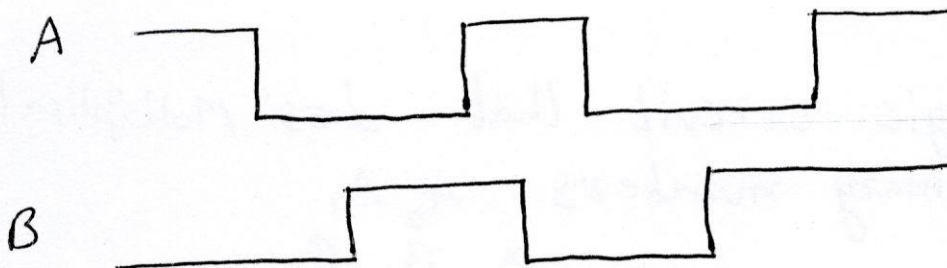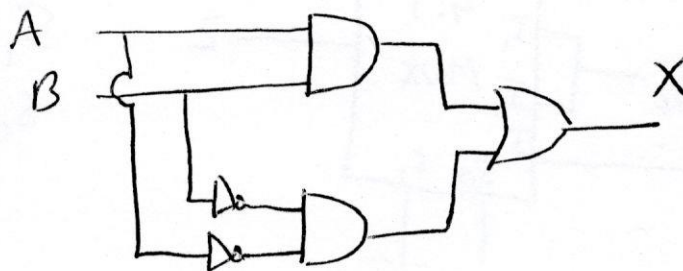- b) Draw the output waveform X for the given circuit




2) perform the following Subtraction


a) $11001 - 10110$ using 1's complement

b) $11011 - 11001$ using 2's complement

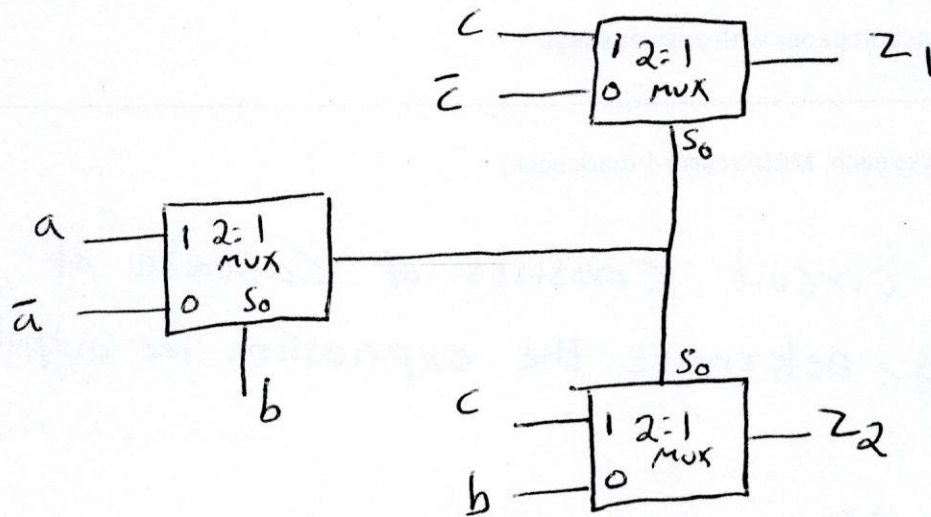3) a) Derive the expression for z_1 & z_2




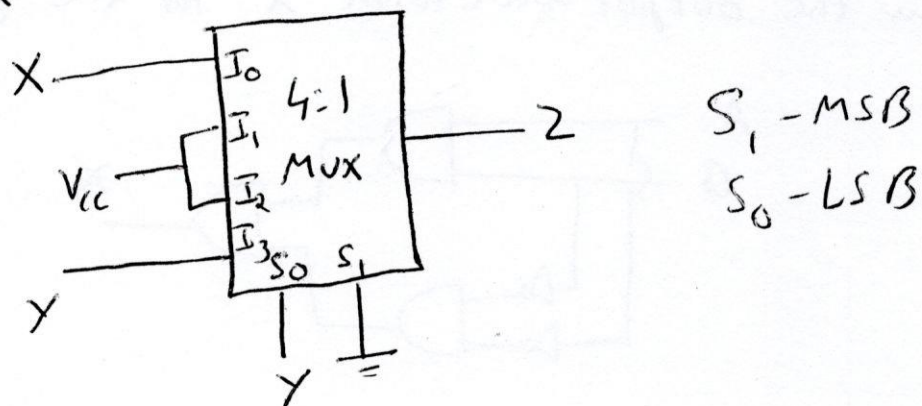b) The output expression for the given 4:1 MUX




4) design a logic circuit that does Multiplication of two bit binary numbers $A_0 A_1$ $\times B_0 B_1$

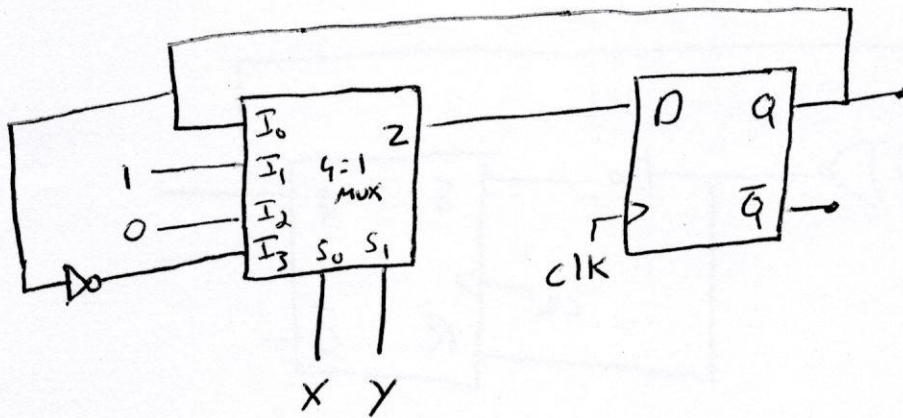5) write the state table & state equations for the given circuit




S_1 - MSB
 S_0 - LSB


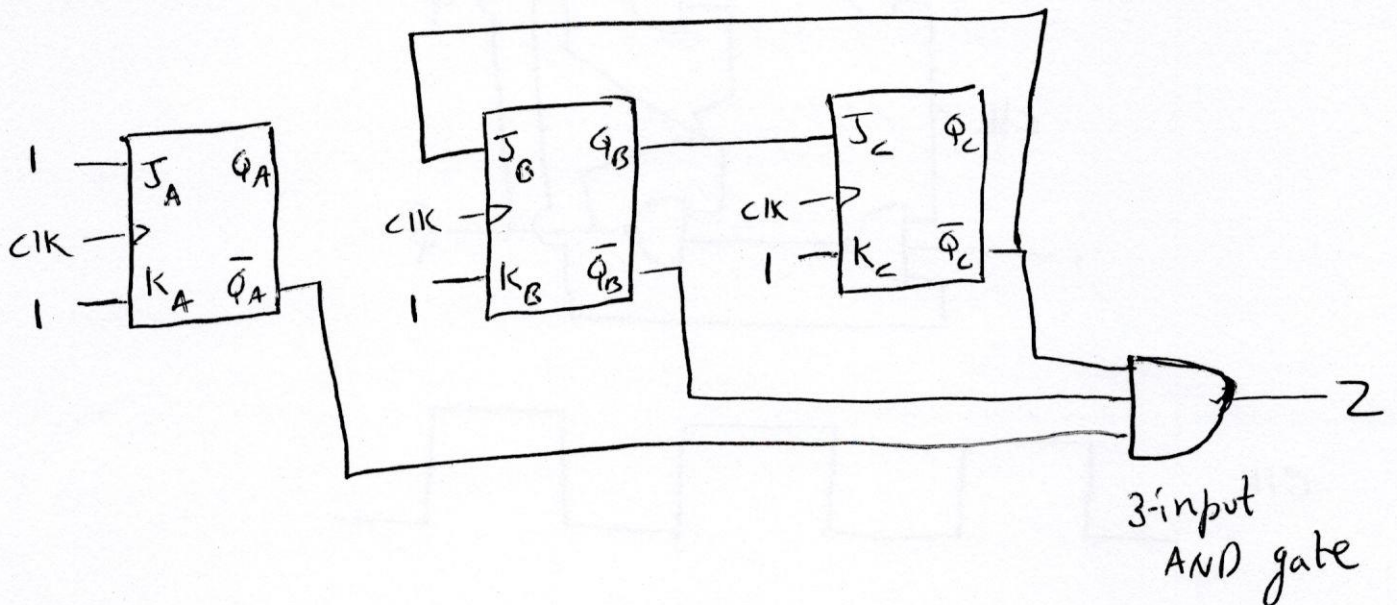
6) For the given circuit, output Z becomes logic one after every "N" clock cycles. Determine the value of N.
Assume initially $Q_A = Q_B = Q_C = 0$.
All the flip flops are connected to common CLK.



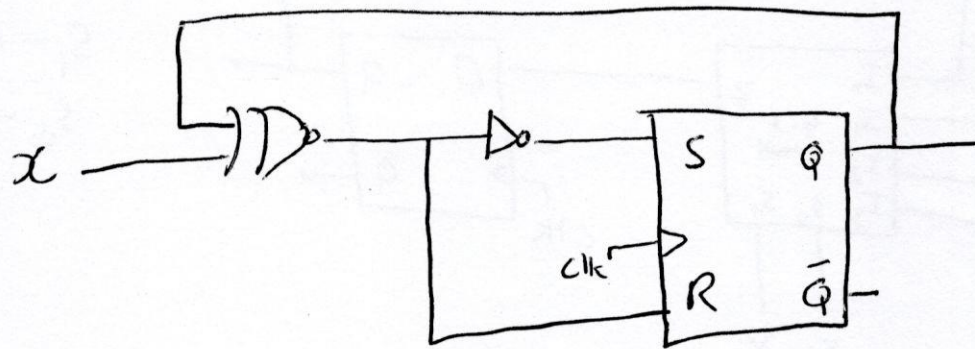7) a) write the state table & state equation for the given circuit



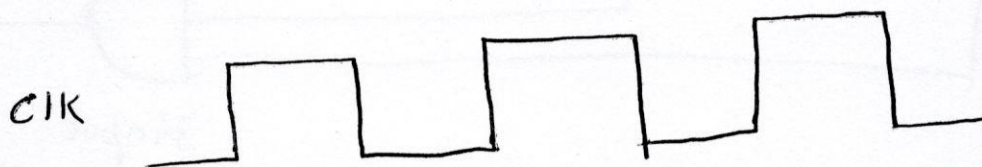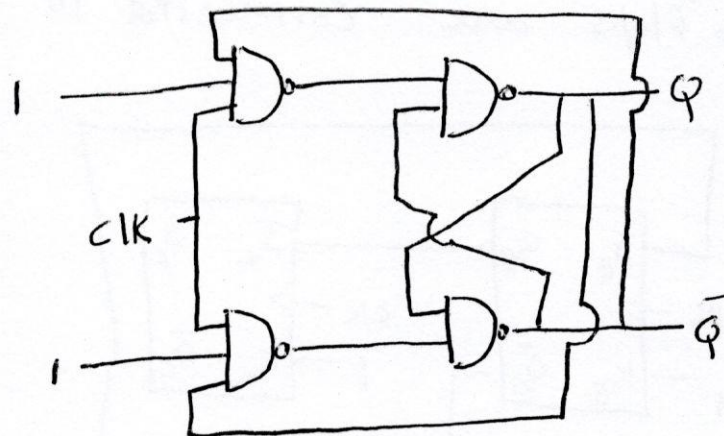b) draw the output waveform at Q for the given circuit. Assume Q is low initially



Part-B


(3)

Solution of first order differential Equation


$$\frac{dx}{dt} + Px = K \text{ is } x(t) = e^{-Pt} \int K e^{Pt} dt + C e^{-Pt}$$

$$\int e^{xt} dt = \frac{1}{x} e^{xt} \quad \frac{d}{dx} e^{ax} = a e^{ax}$$



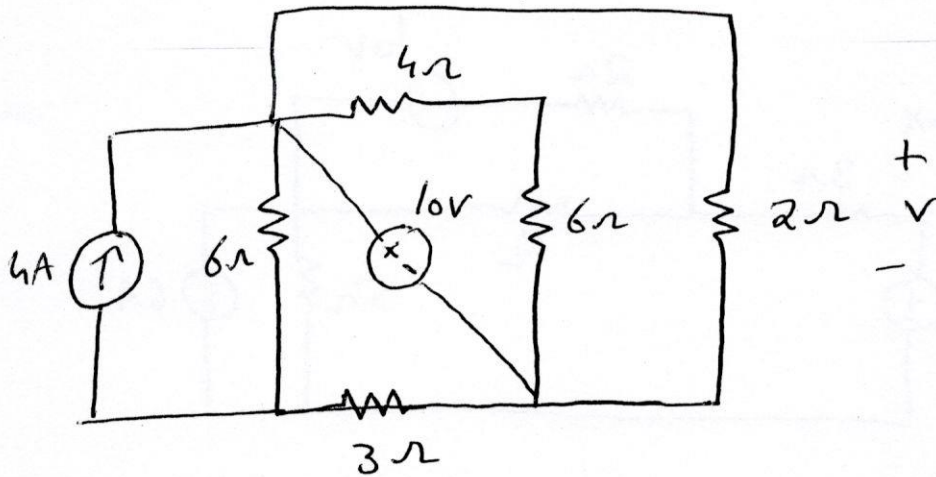
8) using superposition theorem, find voltage drop across 2Ω resistor




9) Find V_0

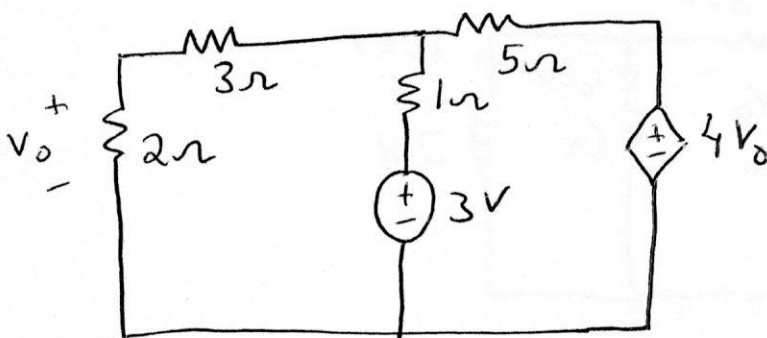

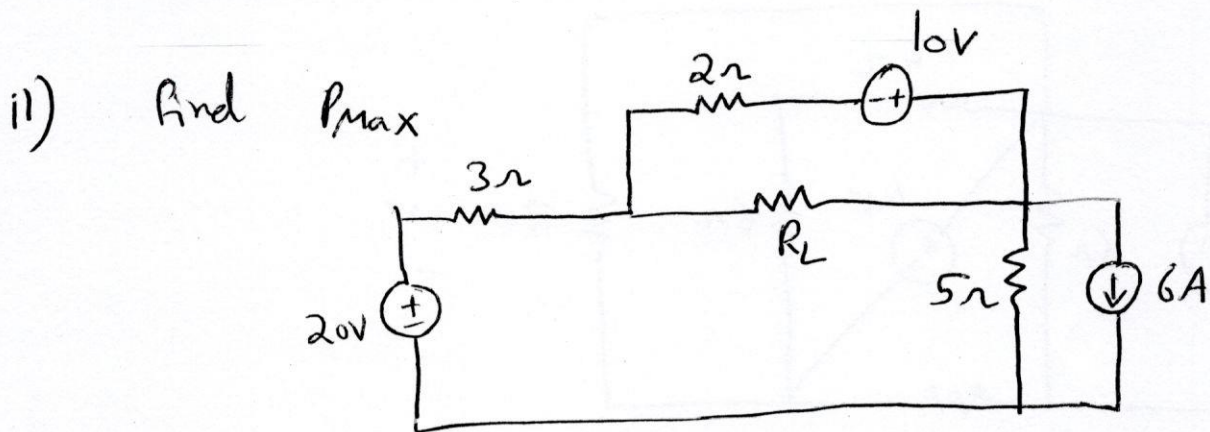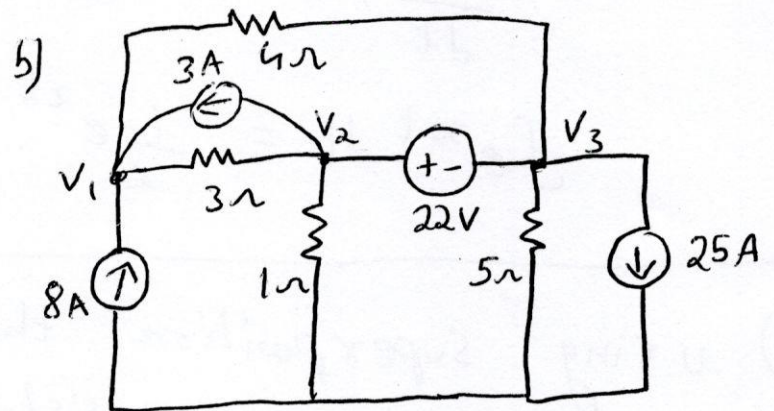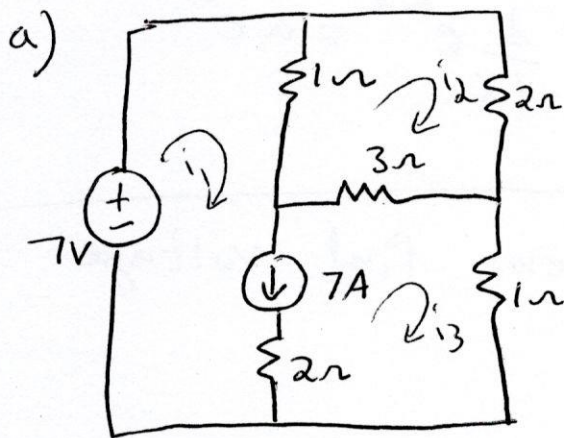
10) Using node/super node and Mesh/Supermesh analysis, write equations for the given circuits



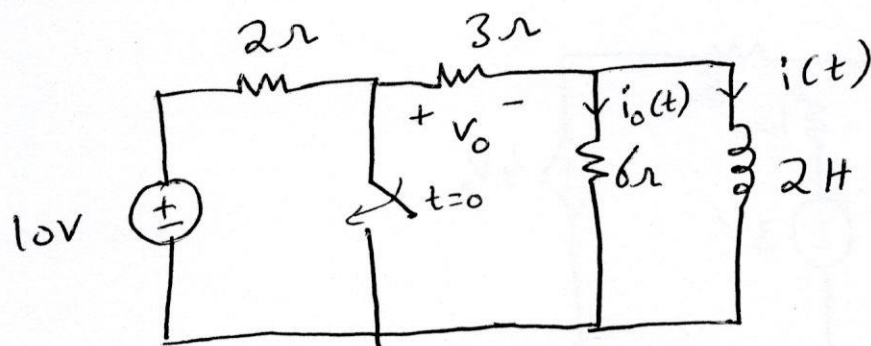
12) Derive expression for $i_o(t)$, $i(t)$ & $V_o(t)$ for $t > 0$. Switch is closed at $t = 0$



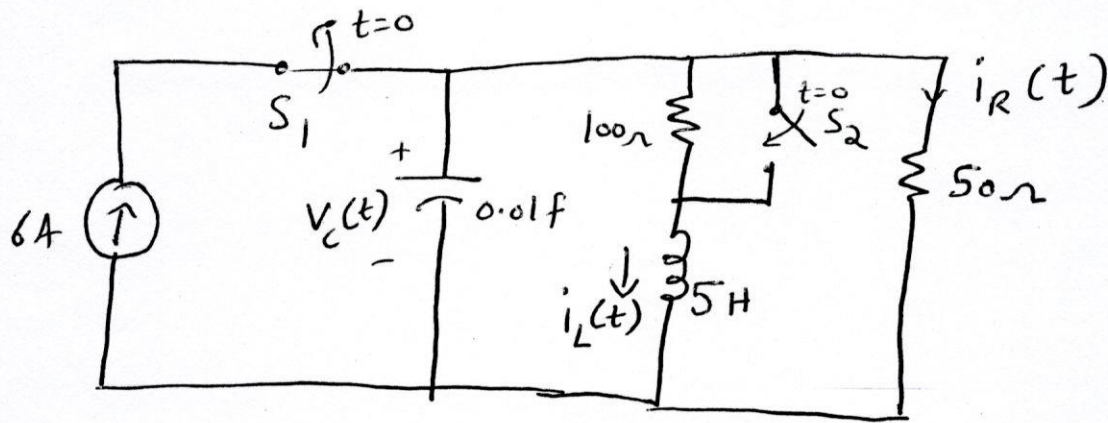
- 13) For the given circuit, find $i_L(0^+)$, $V_C(0^+)$, $i_R(0^-)$, $i_R(0^+)$, $i_L(t)$ for $t > 0$.
At $t=0$, S_1 is opened & S_2 is closed.



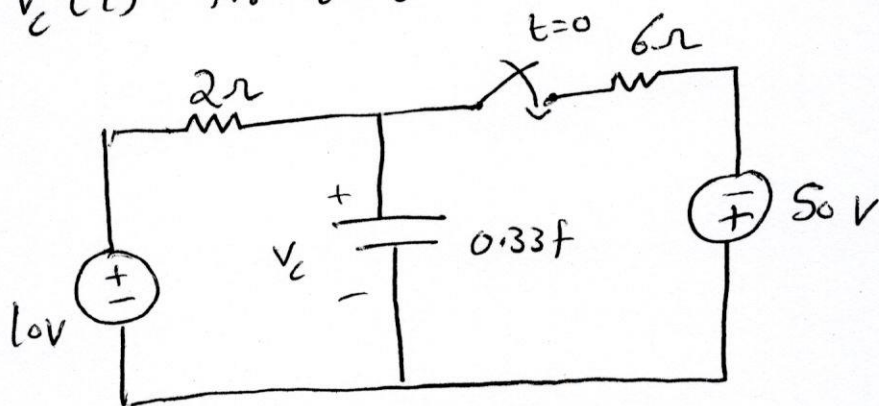- 14) Switch is closed at $t=0$.
Find $V_C(t)$ for $t > 0$.



- 15) Find I

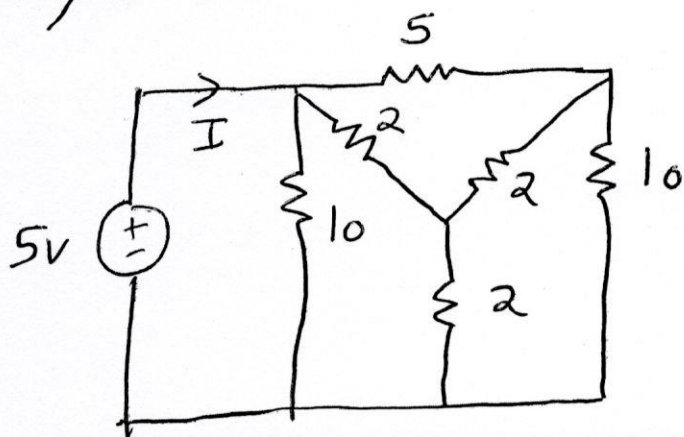

$$R_{ab} = R_a + R_b + \frac{R_a R_b}{R_c}$$


$$R_{bc} = R_b + R_c + \frac{R_b R_c}{R_a}$$

$$R_{ca} = R_a + R_c + \frac{R_a R_c}{R_b}$$

$$R_a = \frac{R_{ab} R_{ac}}{R_{ab} + R_{bc} + R_{ca}} \quad R_b = \frac{R_{bc} R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{ca} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

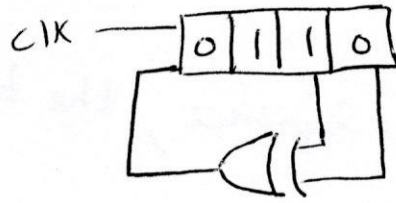1) After three clock pulses, the contents of SIPO shift register will be



- a) 0010 b) 0101 c) 1110 d) 1010

2) If $XY=0$, the $X \oplus Y$ is equal to

- a) $X+Y$ b) $\bar{X} + \bar{Y}$ c) XY d) $\bar{X} \bar{Y}$

3) The Max term designator of the term $\bar{A} + \bar{B} + C + \bar{D}$ in the K-map is


- a) 2 b) 13 c) 10 d) 14

4) If $X\bar{Y} + \bar{X}Y = Z$, then $X\bar{Z} + \bar{X}Z$ is equal to

- a) \bar{X} b) Y c) 0 d) 1

5) In the logic ckt, the redundant gate is

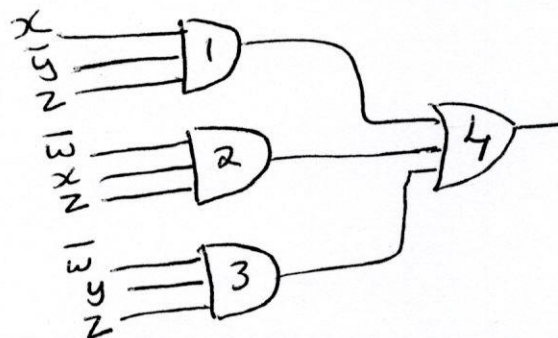- a) 1 ; Gate 1
b) 2 ; Gate 2
c) 3 ; Gate 3
d) 4 ; Gate 4



6) The difference bit output of a half-subtractor is same as

- a) Difference bit output of FS
- b) Sum bit output of HA
- c) Sum bit output of FA
- d) carry bit output of HA.

7) In a 6-bit Johnson counter sequence, the total number of states are

- a) 6
- b) 8
- c) 12
- d) 15

8) The Transient response occurs

- a) only in Resistive ckt
- b) only in capacitive ckt
- c) only in Inductive ckt
- d) Both b & c

9) When a RC circuit connected to a constant voltage at $t=0$, the current passing through the circuit at $t=0^+$ is

- a) Infinite
- b) zero
- c) V/R
- d) RC

10) If the voltage across capacitor $C=200\mu\text{f}$ is $(100-50t)\text{V}$, the current in the capacitor is

- a) -50mA
- b) -10mA
- c) $+15\text{mA}$
- d) $\bar{15}\text{mA}$