

DLD Assignment 2


Due Date: Will be announced in class

- 1) Construct a JK flip flop using a D flip flop, 2:1 MUX and an inverter.
- 2) A sequential circuit with two D flip flops A and B, two inputs, x and y and one output z is specified by the following next state and output equations


$$A(t+1) = xy' + xB, \quad B(t+1) = xA + xB', \quad z = A$$

Build the state table and draw the sequential circuit.

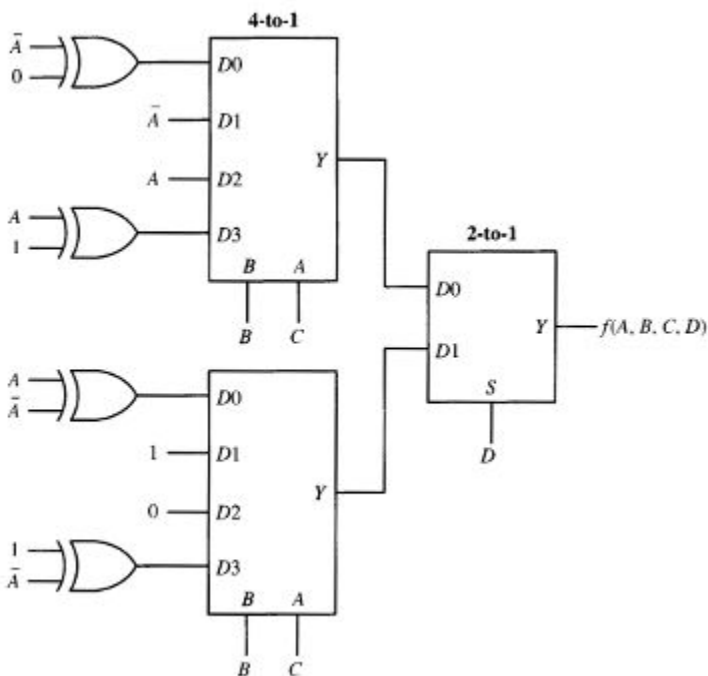
- 3) Find the minterm list of the function $f(A, B, C, D)$




 
- 4) Find the minterm list of the function $f(a, b, c, d)$. FA stands for full adder





5) Draw Q and Q(bar)

 

6) Draw Q and Q(bar)

  

7) Draw Q and Q(bar)

  

8) A sequential circuit has two JK flip flops A and B, two inputs x and y, and one output z. The flip flop input equations and circuit output equations are

$$\begin{aligned} JA &= Bx + B'y' & KA &= B'xy' \\ JB &= A'x & KB &= A + xy' \end{aligned}$$

$$z = Ax'y' + Bx'y'$$

Construct the state table and draw the sequential circuit.

- 9) Design a MOD 10 binary ripple counter that counts from decimal 0 to 9 and repeats itself.
- 10) Design a synchronous UP counter that counts from decimal 0 to 15.
- 11) Design a ripple counter that counts from 11-12 and repeats itself.
- 12) Design a 4 bit binary ripple counter using negative edge triggered D flip flops.
- 13) Design a 4 bit binary ripple UP/DOWN counter using multiplexers.
- 14) Design a four bit shift register with parallel load using D flip flops. There are two control inputs: shift and load. When shift=1 and load=0, the content of the register is shifted by one position. New data are transferred into register when load=1 and shift=0. If both control inputs are equal to 0, the content of the register does not change.
- 15) Draw the logic diagram of a four bit register with four D flip flops and four 4:1 MUX with mode selection inputs s1 and s0. The register operates according to the following function table

<u>S1</u>	<u>S0</u>	<u>Register Operation</u>
0	0	complement the four outputs
0	1	load parallel data
1	0	clear register to zero
1	1	No change

- 16) Design a 4-bit ring and Johnson counter